
Stud	lent's	Name	_
ouu	16111 2	INALLIC	-

Introduction to circuit analysis

Homework 3 – Series Circuit

Instructions:

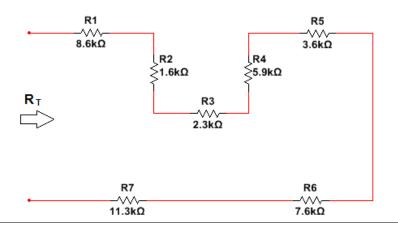- YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT
- All answer must be in engineering notation rounded off to the hundredth
- 1. Find the total resistance R_T of a given circuit




- 2. For the series configuration circuit
 - a. Find the total resistance
 - b. Calculate the source current _____
 - c. Find the voltage across each resistor

 V_{R1} V_{R2} V_{R3}

- d. Calculate power dissipated by the source
- e. Calculate power dissipated by each resistor:


P_{R1} ______P_{R2} ______P_{R3}

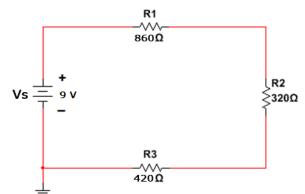


3. Find the voltage source value, E, that will result in the given current:

Find P_{R1}

Find P_T

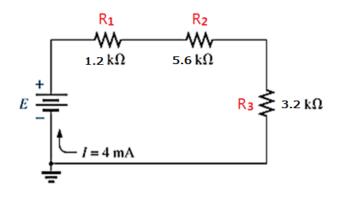

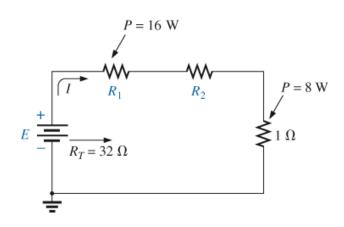

4. Using the provided information, find the unknown quantities for E, V_1 , V_2 , V_3 , R_1 , and R_2


 $E \, \underline{\hspace{1cm}} V_1 \underline{\hspace{1cm}}$


 V_2 _____ V_3 _____

 R_1 _____ R_2 _____

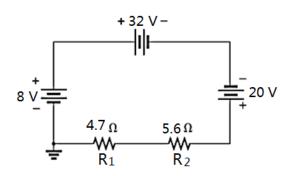5. For the following circuits, determine the current direction and value of the circuit, and the voltage drop through each resistor with their respective voltage polarities:

 $I_{\text{equivalent}} = \underline{\hspace{1cm}} \text{(clockwise or counterclockwise)}$ $V_{\text{R1}} \underline{\hspace{1cm}} V_{\text{R2}} \underline{\hspace{1cm}}$




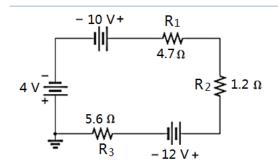


I_{equivalent} = _____(clockwise or counterclockwise)

V_{R1} ______V_{R2} ______V_{R3} _____

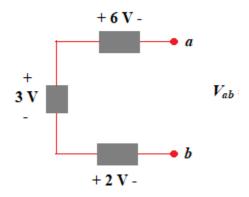6. Find the unknown voltage of the given circuits:



$$V_{ab} = \underline{\hspace{1cm}}$$

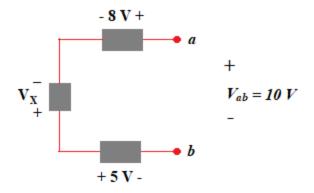

$$V_X =$$